

CDA 3103 Worksheet-8: Adders


Complete the truth-table for the Half-Adder circuit

A	B		Carry	Sum

You should recognize the Carry and Sum as basic logic functions. What are they?

Carry: _____ Sum: _____

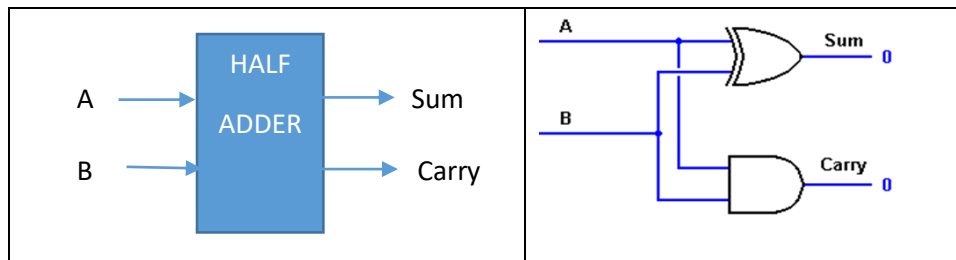Hence, the Half-Adder implementation shown in this logic diagram:



Show how to connect two Half-Adders to form a Full-Adder (You will need an OR-gate)

Hint: $A + B + C_{in} = (A + B) + C_{in}$